

# **Electronics August 2008**

**Achanta Venu Gopal  
Tata Institute of Fundamental Research**

**Research Interests:  
Optical Properties of Semiconductors  
Photonic Crystals – Dielectric and Metallic  
Solid-state Quantum Information Processing**

## **Who am I & how to find me?**

- Member of DCMP&MS
- Office : C-236
- Extn : 2910
  
- Lab : C-225, Ultrafast Spectroscopy Lab
- Extn : 2932
  
- Email : [achanta@tifr.res.in](mailto:achanta@tifr.res.in)
- For any doubts, please feel free to drop an email

## Course Outline

- Circuit Analysis
- Diodes, BJT, FET and their Applications
- Op-Amps, Linear and Non-linear Circuits
- Digital Electronics : Gates, FlipFlops, Counters,..
  
- Introduction to Micro-Processor
- D/A and A/D converters
- Principles of Modern Instrumentation
  - SCA, MCA etc.
- Transducers : Pressure, Temperature, Light, Voltage

## Evaluation

- Home Assignments
- Quizzes
  - Could be surprise – **those who miss gets zero**
- Mid-semester Exam
- Final Exam
  
- Any other suggestions?
  - Term paper, project,...

## **Books to Follow**

- **Mainly,**
  - **Electronic Principles by Malvino and Bates**
  - **Digital Electronics by Leach and Malvino**
  - **Electronic Devices and Circuits by Millman and Halkias**
  
- **Some material from various websites is also used**

## **Detailed Topics to be covered**

## **Circuit Analysis**

- **Passive Components – R, C, L**
- **Circuits with R, C, L combinations**
- **Ohm's Law**
- **Kirchoff's Laws**
- **Joule's Law**
- **Superposition Theorem**
- **Thevenin's Theorem**
- **Norton's Theorem**
- **Millman's Theorem**
- **Reciprocity theorem**
- **Compensation Theorem**
- **Maximum Power Transfer Theorem**
- **Kennelly's Star-Delta Transformations**

## **Diode**

- **Thermionic Diode**
  - Space charge current, thermionic diode vs p-n junction diode
  - Thermionic emission current
- **Semiconductor Diodes :**
  - Bonds in solids
  - Metals, insulators and semiconductors
- **Semiconductors :**
  - Energy bands of semiconductors
  - e-h pairs and carrier densities
  - Conductivity
  - Carrier densities – intrinsic and doped semiconductors
  - Charge densities
  - Impurity
  - Fermi level -- intrinsic and doped semiconductors
  - Diffusion
  - Carrier lifetime
- **Carrier transport : drift, mobility, and diffusion**

- **Processes in Semiconductors:**
  - Excitation in direct and indirect semiconductors
  - Nonradiative processes
- **Carrier recombination and generation**
  - Simple recombination-generation model
  - Band-to-band, Trap-assisted and Surface recombination
- **Generation due to light**
- **Continuity equation**
- **The diffusion equation**
- **The drift-diffusion model**
- **Semiconductor thermodynamics**
  - Thermal equilibrium
  - Fermi energy and Quasi-Fermi energies
  - Energy loss in recombination processes
- **Diffusion current**
- **Tunneling**
- **Metal-Semiconductor contacts**

- **p-n Junctions**
  - Introduction
  - Structure and principle of operation as diode
- **Derivation for barrier width :**
  - solution to Poisson equation with full depletion approximation
  - Flatband diagram
  - Thermal equilibrium
  - The built-in potential at contact
  - Forward and reverse bias
- **p-n diode currents – Solving the Continuity equation for Forward and reverse saturation currents**
- **Capacitance**
  - Junction capacitance
  - Space charge capacitance
  - Diffusion or storage capacitance
- **Diode resistance**
- **p-n diode switching times**
- **Alloy Junction**

- **Reverse bias : Breakdown**
  - General breakdown characteristics
  - Avalanche breakdown
  - Zener breakdown
  - Derivations
  - Surface leakage current
- **Optoelectronic and all-optical devices**
- **Special Purpose Diodes :**
  - Varactor, Zener diode, Tunnel diode, Photodiodes, Schottky diode
- **LEDs :**
  - Introduction to Photoluminescence, Cathodoluminescence, Electroluminescence
  - Complete analysis of LEDs including fabrication technology
  - p-i-n photodiodes
  - Introduction to Photonic crystals and All-optical Diode
- **Application of Diodes :**
  - Rectifiers, clippers, clampers, voltage multipliers, capacitor input filter, choke input filter, peak-to-peak detector, p-i-n structure for single quantum dot spectroscopy
- **Effect of temperature, doping density, confinement (quantum wells, quantum wires, and quantum dots) on band gap**

## BJT

- **Ideal Transistor :**
  - No recombination losses, small diode, no recombination current in depletion layer
- **Bias modes of Transistors :**
  - Detailed analysis of forward active mode, reverse active mode, saturation mode and cut-off mode
- **Ebers-Moll Model**
- **Non-Ideal effects :**
  - base-width modulation, Early effect, change in ideality factor of Collector current, Punch Through effects
  - Current due to recombination in depletion layers
  - High injection effects
  - base spreading resistance
  - temperature dependence and
  - breakdown mechanisms in BJT
- **Load line and Q-point**
- **BJT Technology – history and fabrication technology of BJT, Si IC, Resistor-transistor Logic (RTL)**

## **FET**

- **JFET, D-MOSFET, E-MOSFET**
  - Drain Curves, Transconductance curves
- **Biasing in different regions**
- **Applications to amplifiers, switches and other applications of each of the different FETS**

## **Digital Electronics**

- ***Digital Principles and Applications* by Leach and Malvino**

## Introduction

- Newton's laws, Maxwell's Equations....
- Electronics – involves design and analysis of electronic circuits
  - Based on 2 Kirchoff's laws and Ohm's law
  - These 3 laws give Network theorems like Thevenin, Norton, Superposition, Y-Delta transform,.....
  - what is circuit analysis?

## In the beginning....

- Voltage (Volts,  $v$ ): Work done to move a unit of positive charge between 2 points, from a more negative point (lower potential) to a more positive point (higher potential)
  - Equivalently, it is amount of energy released when a unit charge moves from higher potential to lower potential
  - Voltage is also known as potential difference or electromotive force (emf)
  - A joule of work is needed to move a coulomb of charge through a potential difference of 1 volt

## Current

- **Current (Ampere,  $i$ )** : Rate of flow of electric charge past a point.
  - Current of 1 amp => flow of 1 coulomb of charge per second
  - Conventional current in a circuit flows from a more positive point to a more negative point (Note : electron flow is in opposite direction)

## Power

- **Power (Watts,  $P$ )** : Work per unit time is,  $v.i$  (work/charge x charge/time).
  - $v$  in volts,  $i$  in amps, gives Power in Watts
  - 1 Watt = 1Joule/sec
  - Power goes into heat (usually), mechanical energy (motors), radiated energy (lamps, transmitters), or stored energy (batteries, capacitors)

## **Voltage and Current Sources**


- **Voltage Source** : A perfect one can maintain a fixed voltage drop across its terminals, regardless of load resistance.
- **Current Source** : It can maintain constant current through the external circuit, regardless of load resistance or applied voltage.

## **Heart of Electronics**

- **I vs V characteristics** :
  - To design and develop gadgets with useful I-V characteristics
  - Eg., Resistors, capacitors, diodes, transistors,..
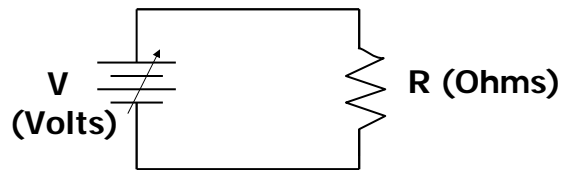
## A simple Circuit


- Resistor : Current is proportional to Voltage -- Ohm's law :  $v=i R$  or  $R= v/i$




Imagine what a simple circuit like this can do?  
What could be happening here?

## Resistors in Series and Parallel

- Resistances in Series :

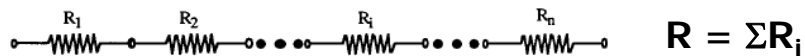

- Resistances in Parallel :

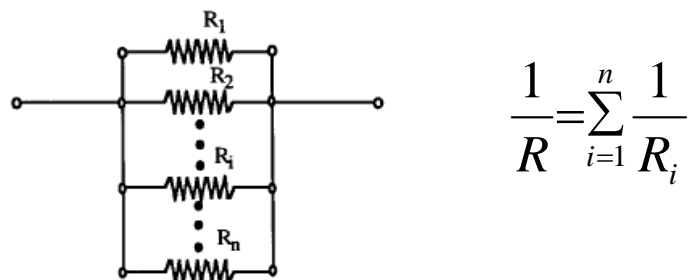

## Colour Code for Resistors

| Color   | First Band | Second Band | Third Band    | Fourth Band Tolerance, % |
|---------|------------|-------------|---------------|--------------------------|
| Black   | 0          | 0           | 1             |                          |
| Brown   | 1          | 1           | 10            |                          |
| Red     | 2          | 2           | 100           |                          |
| Orange  | 3          | 3           | 1,000         |                          |
| Yellow  | 4          | 4           | 10,000        |                          |
| Green   | 5          | 5           | 100,000       |                          |
| Blue    | 6          | 6           | 1,000,000     |                          |
| Violet  | 7          | 7           | 10,000,000    |                          |
| Gray    | 8          | 8           | 100,000,000   |                          |
| White   | 9          | 9           | 1,000,000,000 |                          |
| Gold    |            |             | 0.1           | 5%                       |
| Silver  |            |             | 0.01          | 10%                      |
| No band |            |             |               | 20%                      |



## Kirchoff's Laws

- **Kirchoff's Voltage Law** : The sum of voltage drops around any loop in any circuit is zero :  
**Conservation of Energy**
  - Things placed in parallel have same voltage drop across them
- **Kirchoff's Current Law** :The sum of currents flowing into each node of a circuit is equal to the sum of currents flowing out of that node :  
**Conservation of charge**
  - For a series circuit, the current is same everywhere
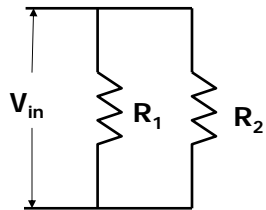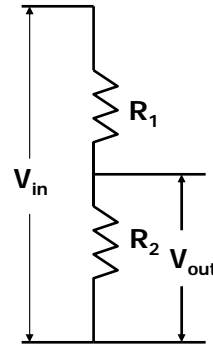
## Resistor combination

$$I = \frac{V_{in}}{R_1 + R_2}$$

$$V_{out} = IR_2 = \frac{R_2}{R_1 + R_2} V_{in}$$



What does this circuit do?

## Use of Kirchoff's Laws

- Solved examples

# Thumb Rules in Using Ohm's Law

For series circuits:

|   | R <sub>1</sub> | R <sub>2</sub> | R <sub>3</sub> | Total   |       |
|---|----------------|----------------|----------------|---------|-------|
| E | →              | →              | →              | → Add   | Volts |
| I | →              | →              | →              | → Equal | Amps  |
| R | →              | →              | →              | → Add   | Ohms  |
| P | →              | →              | →              | → Add   | Watts |

$$E_{\text{total}} = E_1 + E_2 + E_3$$

$$I_{\text{total}} = I_1 = I_2 = I_3$$

$$R_{\text{total}} = R_1 + R_2 + R_3$$

$$P_{\text{total}} = P_1 + P_2 + P_3$$

For parallel circuits:

|   | R <sub>1</sub> | R <sub>2</sub> | R <sub>3</sub> | Total      |       |
|---|----------------|----------------|----------------|------------|-------|
| E | →              | →              | →              | → Equal    | Volts |
| I | →              | →              | →              | → Add      | Amps  |
| R | →              | →              | →              | → Diminish | Ohms  |
| P | →              | →              | →              | → Add      | Watts |

$$E_{\text{total}} = E_1 = E_2 = E_3$$

$$I_{\text{total}} = I_1 + I_2 + I_3$$

$$R_{\text{total}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$P_{\text{total}} = P_1 + P_2 + P_3$$

## Capacitor

- Electronic component that stores energy in the form of electrostatic field.
  - Two conducting plates separated by an insulating material

- $C = Q/V$  (Charge/Voltage)

- Capacitors in series :

$$\frac{1}{C} = \sum_{i=1}^n \frac{1}{C_i}$$



- Capacitors in parallel :

$$C = \sum_{i=1}^n C_i$$

- Applications : Filters, block dc, pass ac, bypass, shift phase, isolate, store energy, suppress noise,...
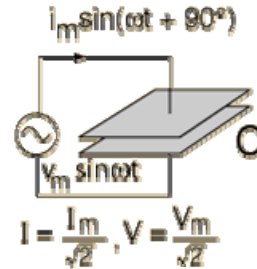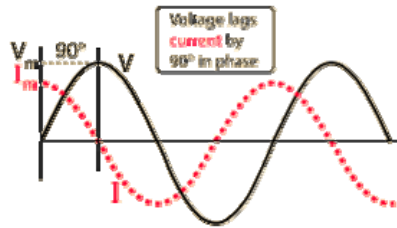
## Capacitor-AC Response

- Charging of capacitor :  $Q = CV(1 - e^{-t/RC})$ ,  $\tau = RC$



- Impedance (Z) : Due to phase difference between resistive and capacitor and inductor components
- Capacitive Reactance:  $X_C = \frac{1}{\omega C}$

## Inductor

- An electronic component that stores energy in the form of magnetic field.
  - Wire loop or coil



- Inductors in series : 
$$L = \sum_{i=1}^n L_i$$

- Inductors in parallel : 
$$\frac{1}{L} = \sum_{i=1}^n \frac{1}{L_i}$$

- Applications : tuners, filters, transformers, ...
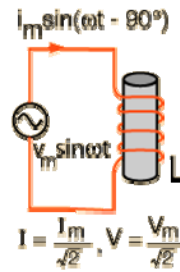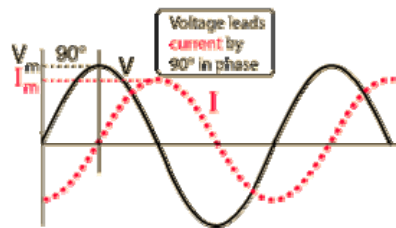
## Inductor – AC Response

Inductor Current build-up :  $I = (V/R)(1 - e^{-t/(L/R)})$ ,  $\tau = L/R$




- Inductive Reactance:  $X_L = \omega L$


## Combination of R,C,L
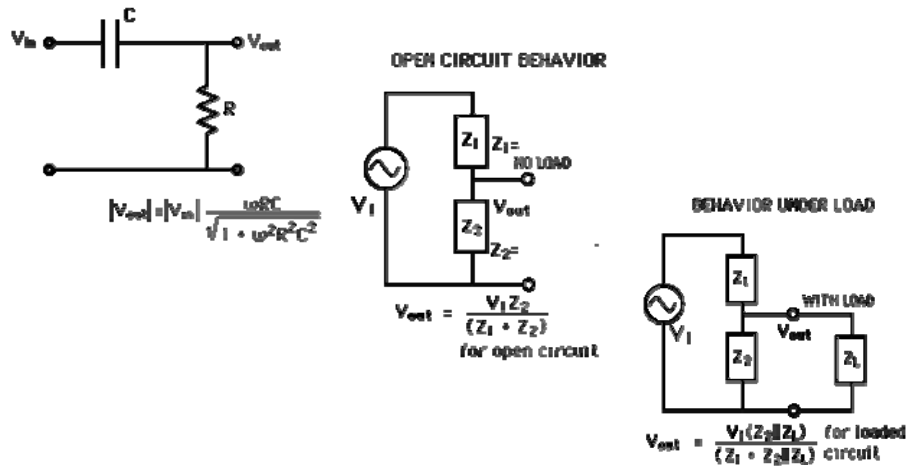
## RC – High Pass Filter Circuit

- Capacitive reactance decreases with frequency
- Passes high frequency components




## RC – Low Pass Filter Circuit

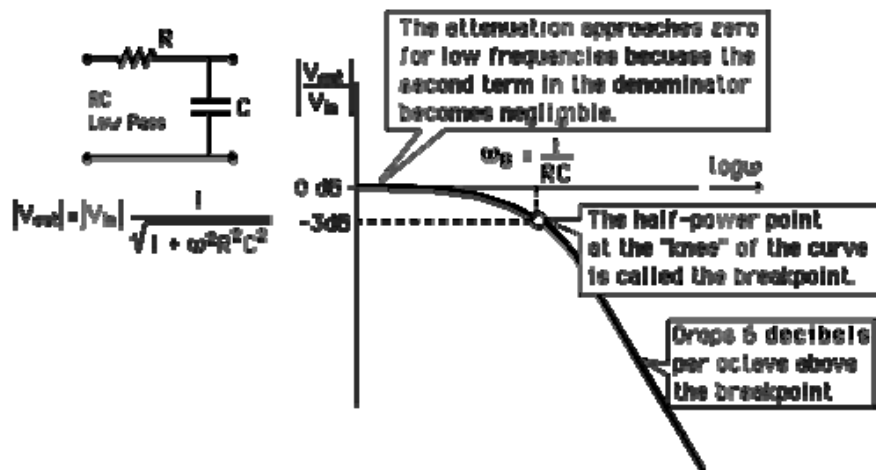

## LR Circuit

- Check what happens

## LC Circuit

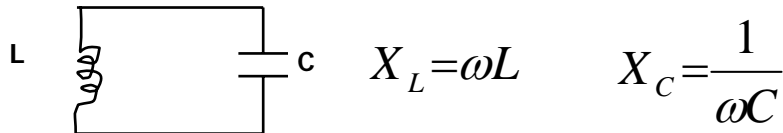

$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$

At Resonant Frequency ( $\omega_r$ ),  $X_L = X_C$       $\omega_r = \frac{1}{\sqrt{LC}}$

For  $\omega < \omega_r$ ,  $X_L < X_C$  -- Circuit is Capacitive

For  $\omega > \omega_r$ ,  $X_L > X_C$  -- Circuit is Inductive

**In Series :**  $X_C$  leads by  $90^\circ$  while  $X_L$  lags by  $90^\circ$

--At  $\omega_r$  they cancel each other and current is maximum

-- Series resonant ckt provides voltage magnification

**In Parallel:**  $X_L = X_C \Rightarrow$  branch currents equal and opposite

--Current in main line is minimum

-- Parallel resonant ckt provides current magnification

## LCR Circuit

